

Universidade de Aveiro

Mestrado em Engenharia de Computadores e Telemática Arquitecturas de Alto Desempenho

Assignment 1 – Hamming codes

ua

Academic year 2021/2022

Design a digital circuit, called the *encoder*, which performs the encoding for a [15,11] Hamming code (either combinatorial or bit-serial). Design also a digital circuit, called the *decoder*, which detects and corrects a 1-bit error on the received code word (either combinatorial or bit-serial).

The assignment entails that some investigation should be made on finding the best possible algorithms for the implementation of the operations.

GRADING

- full specification of the *encoder* and proof of correctness of its design by VHDL simulation in Quartus 14 valores
- full specification of the *decoder* and proof of correctness of its design by VHDL simulation in Quartus 17 valores
- there should always be a combinatorial and a bit-serial implementation.

DELIVARABLES

- an archive, named HAM_T\$G#.zip (where \$, equal to 1, ..., 4, means the lab number and #, equal to 1, ..., 8, means the group number), of the VHDL files of your solution in directories named, encoder and decoder, respectively
- a pdf file, named present.pdf, up to 6 power point like pages, where the main ideas of the design and the conclusions of the work are presented.

DEADLINE

• December, 8, at midnight.